
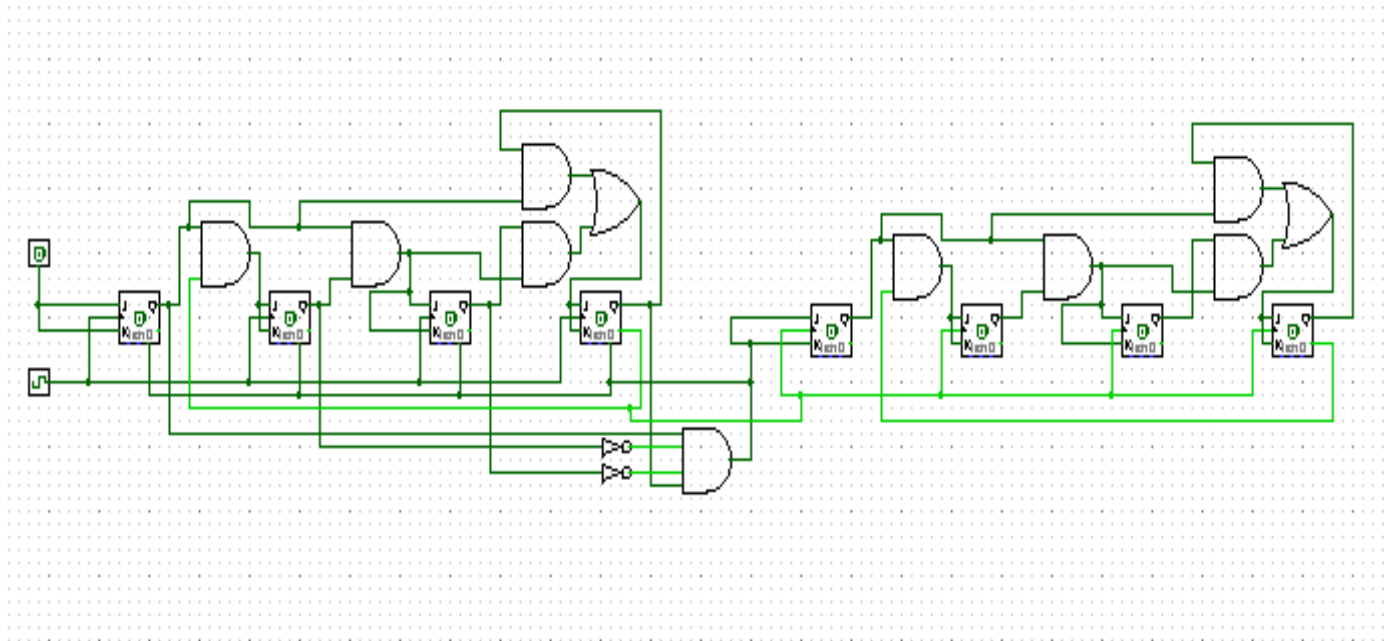


WEEK 4 CIRCUITS


Digital clock:

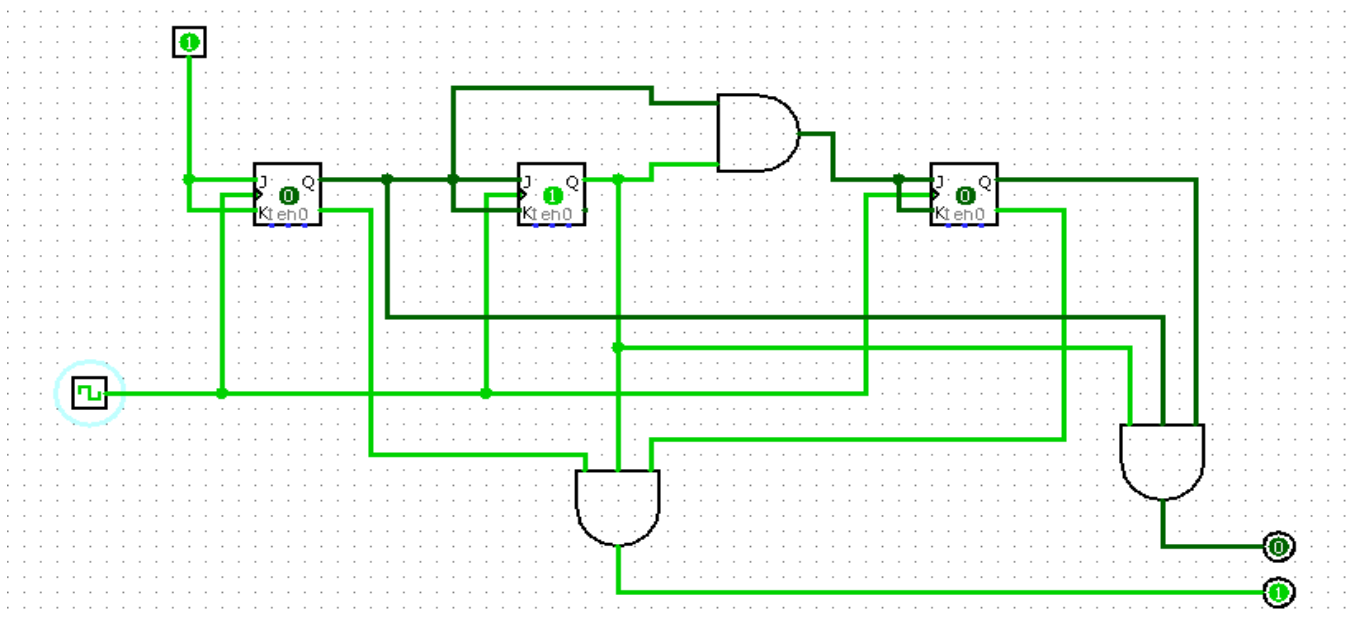

A 3-bit counter with active-HIGH decoding of count 2 and count 7:



A synchronous BCD decade counter:

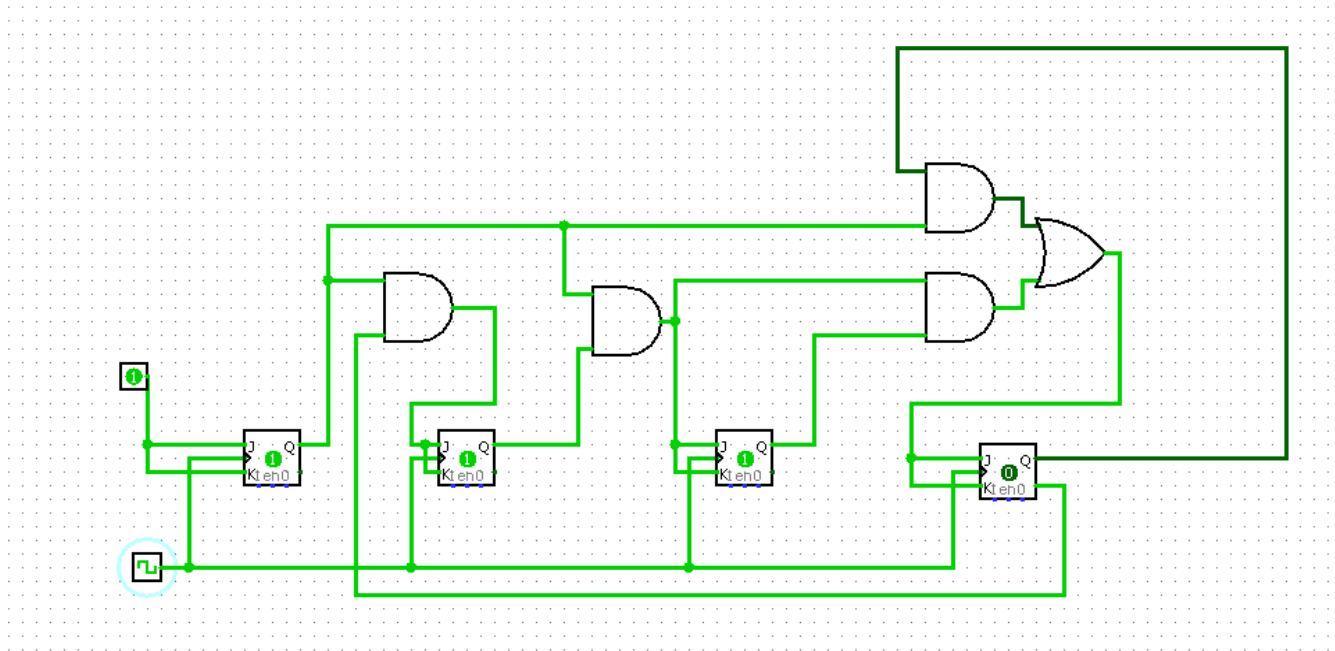

Counter decoding:

